

ΜΗΧΑΝΙΚΩΝ Η/Υ ΚΑΙ ΠΛΗΡΟΦΟΡΙΚΗΣ

# ΠΡΩΤΗ ΕΡΓΑΣΤΗΡΙΑΚΗ ΑΣΚΗΣΗ

#### ΠΡΩΤΟ ΕΡΩΤΗΜΑ :

 

 



# Πίνακας Αληθείας

a	b	С	d	F
0	0	0	0	0
1	0	0	0	0
0	1	0	0	0
1	1	0	0	1
0	0	1	0	0
1	0	1	0	0
0	1	1	0	0
1	1	1	0	1
0	0	0	1	0
1	0	0	1	0
0	1	0	1	0
1	1	0	1	1
0	0	1	1	1
1	0	1	1	1
0	1	1	1	1
1	1	1	1	1

#### ΔΕΥΤΕΡΟ ΕΡΩΤΗΜΑ:

### Το κύκλωμα:

 

 


# Πίνακας Αληθείας:

А	С	F
0	0	0
1	0	1
0	1	1
1	1	1
0	0	0
1	0	1
0	1	1
1	1	1


Απλοποίηση της F με άλγεβρα Boole:

Η συνάρτηση είναι:

F = [(ab)'\*(cd)']' = ab+cd

 


Είναι η OR

 


είναι η απλοποιημένη μορφή του παραπάνω κυκλώματος

### **TPITH EPΩTHMA:**

 

Type ID Message

- 332102 Design is not fully constrained for setup requirements
- 332102 Design is not fully constrained for hold requirements
- > ① Quartus II 64-Bit TimeQuest Timing Analyzer was successful. 0 errors, 4 warnings
- \*
- > (1) Running Quartus II 64-Bit EDA Netlist Writer
  - Command: quartus eda --read settings files=off --write settings files=off Question3 -c Question3
- 1 204026 Generated files "Question3.vho", "Question3 fast.vho", "Question3 vhd.sdo" and "Question3 vhd fast.sdo" in directory "C:/altera/13.0sp1/digital di/
- > (1) Quartus II 64-Bit EDA Netlist Writer was successful. 0 errors, 0 warnings
- 1293000 Quartus II Full Compilation was successful. 0 errors, 12 warnings

 

## Πίνακας αληθείας :

х	У	F
0	0	0
1	0	1
0	1	1
1	1	1

# Απλοποίηση της F με αλγεβρα Boole:

$$\mathbf{F} = xy + x'y + xy' \leftrightarrow$$


$$F=x(y+y')+x'y\longleftrightarrow$$


$$F = x + x'y \leftrightarrow$$


$$F = (x+x') + (x+y) \leftrightarrow$$

$$F = x+y$$

 Και η απλοποιημένη μορφή του κυκλώματος είναι :



 

 

### Πίνακας αληθείας :

х	У	F
0	0	0
1	0	1
0	1	1
1	1	1

ΤΕΛΟΣ το κόστος στο αρχικό κύκλωμα : 4 πύλες και 9 διασυνδέσεις

Ένω του απλοποιημένου κυκλώματος : 1 πύλη και 2 διασυνδέσεις